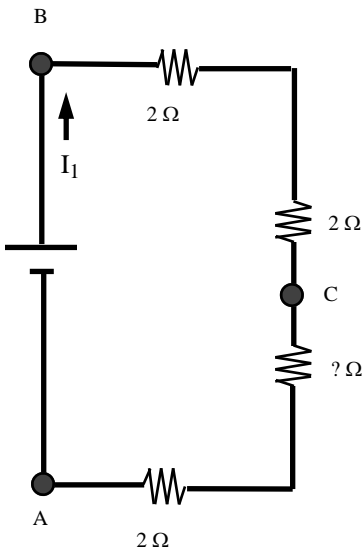


## Test 4 Circuits Review

1.



$$V_{AB} = 50 \text{ V}$$


$$V_{CB} = 20 \text{ V}$$

$$V_{AC} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$R_T = \underline{\hspace{2cm}}$$

2.

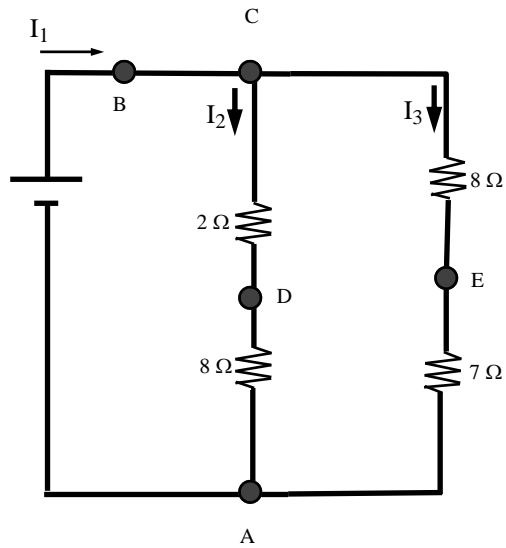

$$V_{AB} = \underline{\hspace{2cm}}$$

$$V_{CB} = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

$$V_{AE} = \underline{\hspace{2cm}}$$

$$V_{AD} = \underline{\hspace{2cm}}$$


$$I_1 = 15 \text{ A}$$

$$I_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}}$$

$$R_T = \underline{\hspace{2cm}}$$

3.

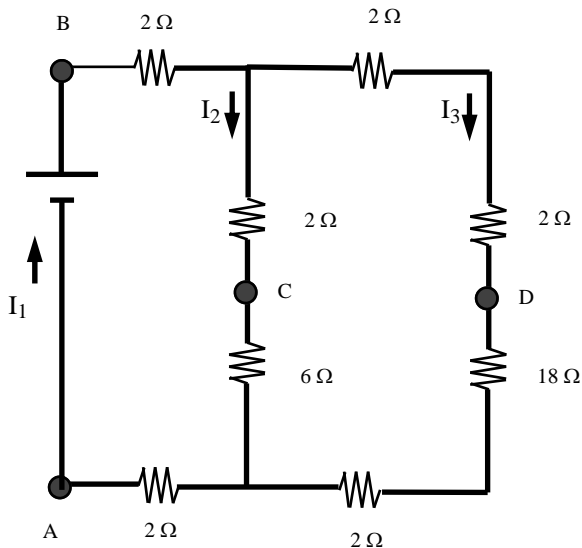

$$V_{AB} = \underline{\hspace{2cm}}$$

$$V_{AC} = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

$$V_{AD} = \underline{\hspace{2cm}}$$

$$V_{DB} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$I_2 = 6 \text{ A}$$

$$I_3 = \underline{\hspace{2cm}}$$

$$R_T = \underline{\hspace{2cm}}$$

Review HW 4.1

You need to be able to solve problems using the following formulas:

$$Q = It \quad V = IR \quad P = E/t \quad P = VI \quad P = I^2R \quad P = V^2/R$$

Review HW 4.2, HW 4.3, HW 4.4 and HW 4.5

You will need to be able to analyze series, parallel and combination circuits. You **MUST** draw and label all current and voltage arrows in order to receive full credit.