

1. The compressor on an air conditioner draws 90 A when it starts up. If the start up time is about 0.5 seconds, how much charge passes a cross-sectional area of the circuit in this time?

$$I = 90 \text{ A}$$

$$t = 0.5 \text{ s}$$

$$Q = ?$$

$$Q = I \cdot t$$

$$= (90)(0.5)$$

$$= \underline{\underline{45 \text{ C}}}$$

45 C

2. A circuit contains a 9 V battery and a 500 Ω Resistor. What is the current in this circuit?

$$V = 9 \text{ V}$$

$$R = 500 \Omega$$

$$I = ?$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{9}{500}$$

0.018 A

3. A person notices a mild shock if the current along a path through the thumb and index finger exceeds 80 μA. What is the maximum allowable voltage without shock if your dry skin resistance is 4.0 E 5 Ω? What is the maximum allowable voltage without shock if your wet skin resistance is 2000 Ω?

$$I = 80 \times 10^{-6} \text{ A}$$

$$R_d = 4.0 \times 10^5 \Omega$$

$$R_w = 2000 \Omega$$

$$V_d = ?$$

$$V_w = ?$$

$$V = IR$$

$$V_d = (80 \times 10^{-6})(4.0 \times 10^5)$$

$$V_d = 32 \text{ V}$$

$$V_w = (80 \times 10^{-6})(2000)$$

$$V_w = 0.16 \text{ V}$$

32 V

0.16 V

4. All electrical devices are required to have an identifying plate that specifies their electrical characteristics. For example, the plate on an iron might state that the iron carries a current of 6 A when connected to a 120 V source. What is the resistance in the iron?

$$I = 6 \text{ A}$$

$$V = 120 \text{ V}$$

$$R = ?$$

$$V = IR$$

$$R = \frac{V}{I} = \frac{120}{6} = \underline{\underline{20 \Omega}}$$

20 Ω

5. A typical color TV draws about 2.5 A when connected to a 120 V source. What is the overall resistance of the TV set?

$$I = 2.5 \text{ A}$$

$$V = 120 \text{ V}$$

$$R = ?$$

$$V = IR$$

$$R = \frac{V}{I} = \frac{120 \text{ V}}{2.5 \text{ A}}$$

48 Ω

6. To charge the battery used for a boat trolling motor, a charger provides 4.5 A for 7 hours. How much charge passes through the battery?

$$I = 4.5 \text{ A}$$

$$t = 7(3600) \text{ s}$$

$$Q = ?$$

$$Q = I \cdot t$$

$$Q = (4.5)(7)(3600)$$

$$Q = 113,400$$

113,400 C

7. The sticker on a portable CD player says it draws 300 mA of current at 9 V. What power does it dissipate?

$$I = 0.3 \text{ A}$$

$$V = 9 \text{ V}$$

$$P = ?$$

$$P = V \cdot I$$

$$P = (9)(0.3) = 2.7 \text{ W}$$

2.7 W

8. How much charge runs through a 100 W light bulb connected to a 120 V source for one hour?

$$Q = ?$$

$$P = 100 \text{ W}$$

$$V = 120 \text{ V}$$

$$t = 3600 \text{ s}$$

$$P = V \cdot I$$

$$Q = I \cdot t$$

$$I = \frac{Q}{t}$$

$$P = \frac{V \cdot Q}{t}$$

$$Q = \frac{P \cdot t}{V} = \frac{(100)(3600)}{120}$$

3000 C

9. An Ipod draws 0.900 Amps at 3 Volts. How much resistance does the Ipod have?

$$I = 0.900 \text{ A}$$

$$V = 3 \text{ V}$$

$$R = ?$$

$$V = IR$$

$$R = \frac{V}{I} = \frac{3}{0.9}$$

3.3 Ω

10. A 1500 watt electric penguin draws 83 mA of current. What is the resistance of the penguin?

$$P = 1500 \text{ W}$$

$$I = 0.083 \text{ A}$$

$$R = ?$$

$$P = I^2 R$$

$$R = \frac{P}{I^2} = \frac{1500}{(0.083)^2} = 217738.42 \Omega$$

218 k Ω

11. If 5 mA of current runs through a wire in a CD player, how long would it take for 1.25×10^{19} electrons to pass a point in this wire? (1 electron = 1.6×10^{-19} Coulombs)

$$I = 0.005 \text{ A}$$

$$\#e = 1.25 \times 10^{19}$$

$$t = ?$$

$$Q = (1.25 \times 10^{19})(1.6 \times 10^{-19})$$

$$Q = I \cdot t$$

$$t = \frac{Q}{I} = \frac{(1.25 \times 10^{19})(1.6 \times 10^{-19})}{0.005}$$

400 s

12. In a particular television tube, the beam current is 60 mA. How long does it take for 3.75×10^{14} electrons to strike the screen?

$$I = 0.06 \text{ A}$$

$$Q = (3.75 \times 10^{14})(1.6 \times 10^{-19})$$

$$t = ?$$

$$Q = I \cdot t$$

$$t = \frac{Q}{I} = \frac{(3.75 \times 10^{14})(1.6 \times 10^{-19})}{0.06}$$

0.001 s

13. Find the current in the following devices when they are connected across a potential difference of 120 V.

- a. A hot plate with a resistance of 48 Ω .
- b. A microwave oven with a resistance of 20 Ω .

$$V = 120 \text{ V}$$

$$I_a = ?$$

$$I_b = ?$$

$$R_a = 48 \Omega$$

$$R_b = 20 \Omega$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I_a = \frac{120}{48}$$

$$I_b = \frac{120}{20}$$

$$= 2.5 \text{ A}$$





$$= 6 \text{ A}$$





2.5 A

6 A


HW 4.2 Series Circuits
Copying is not allowed

Per _____ Name _____

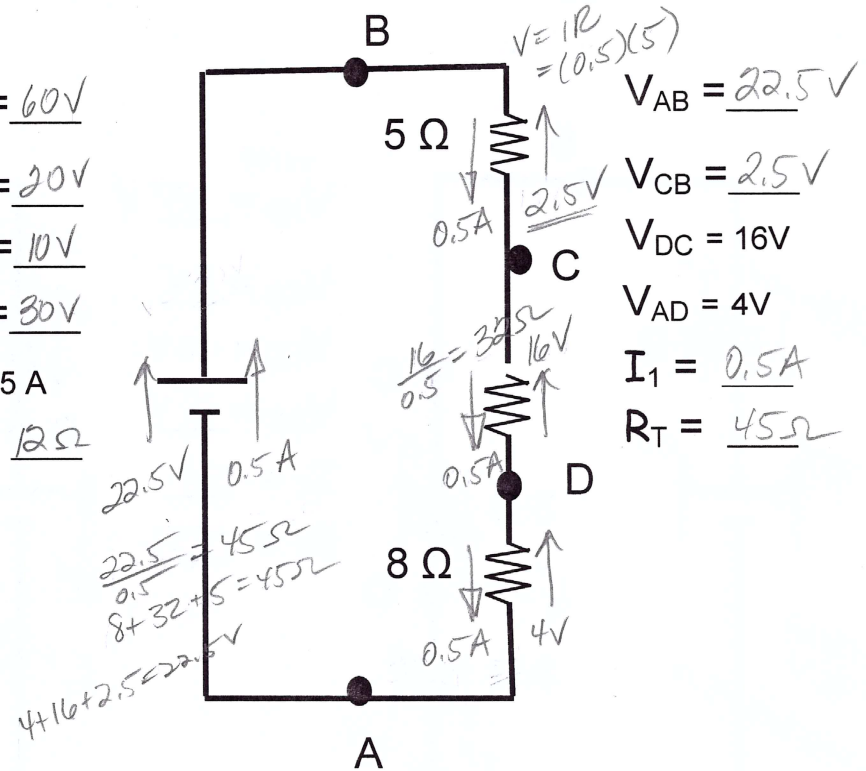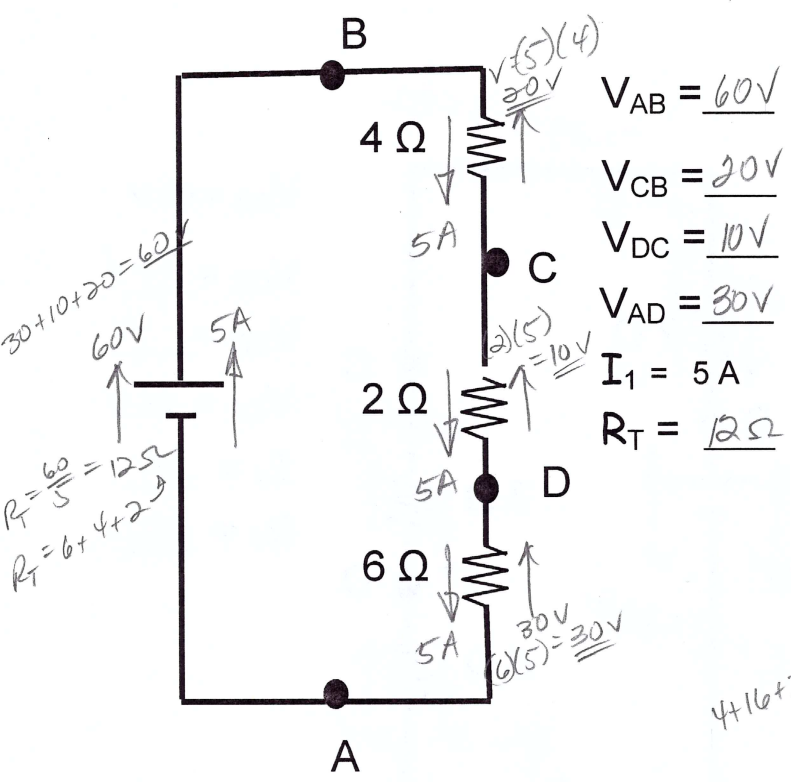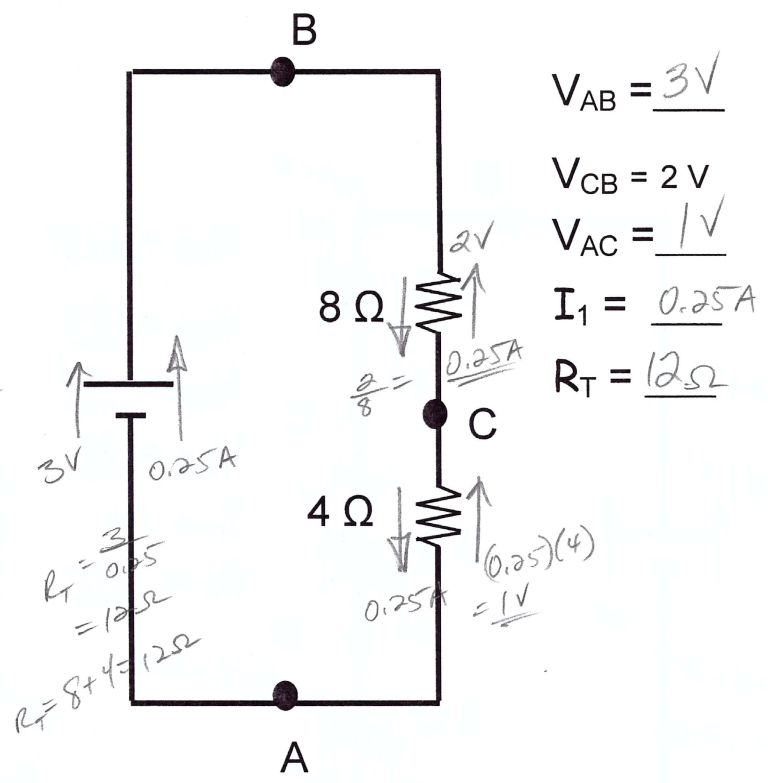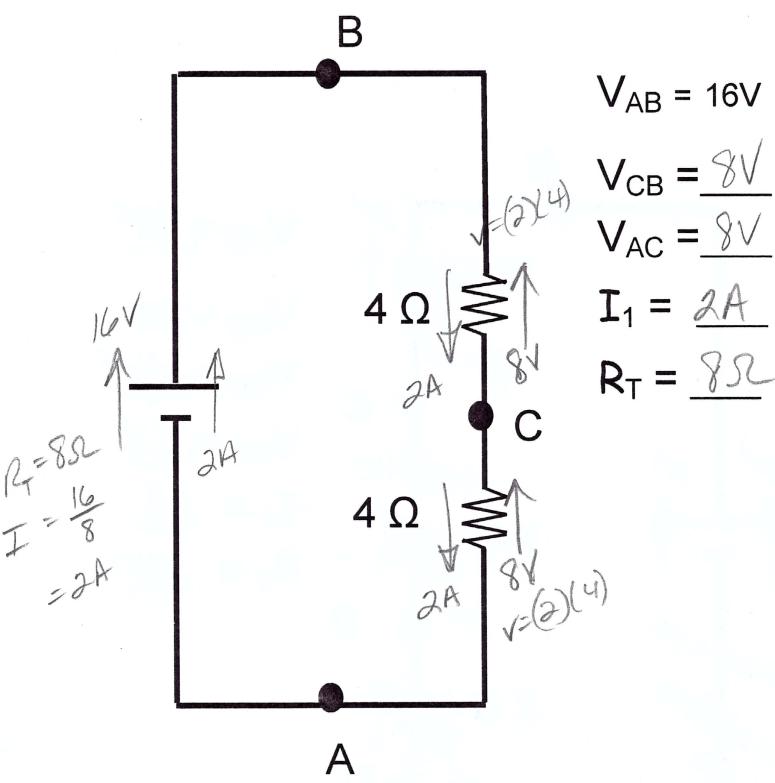

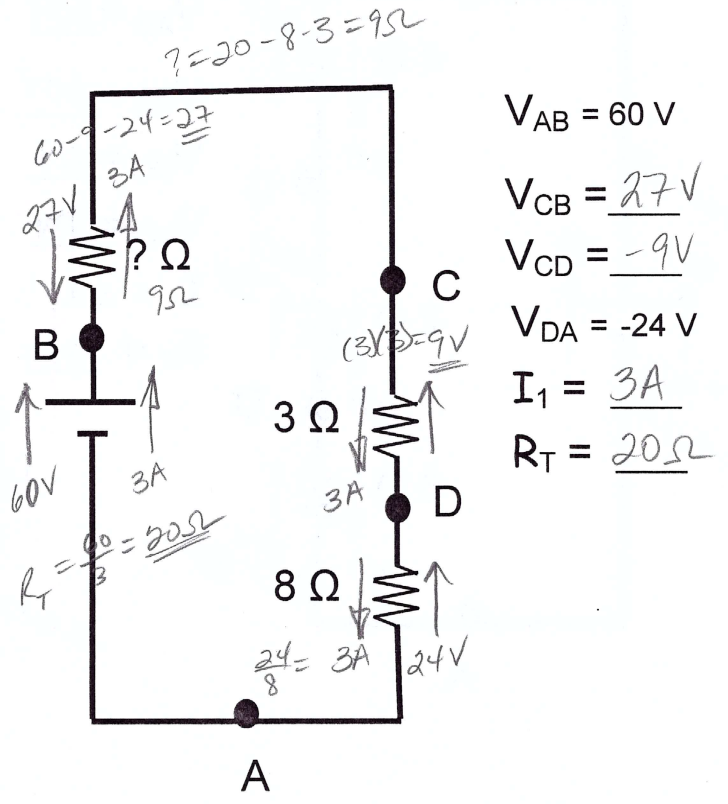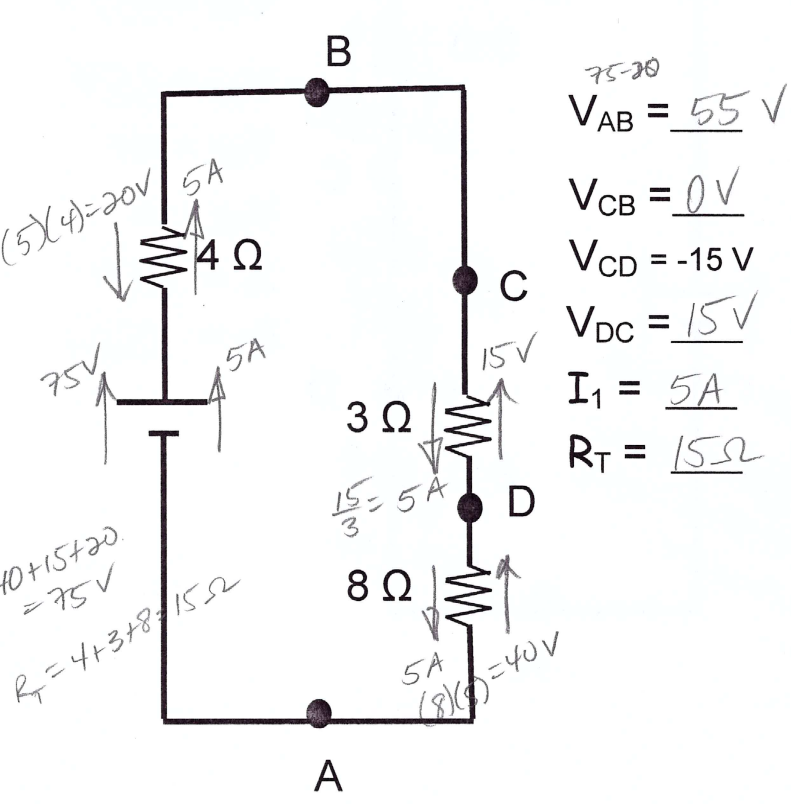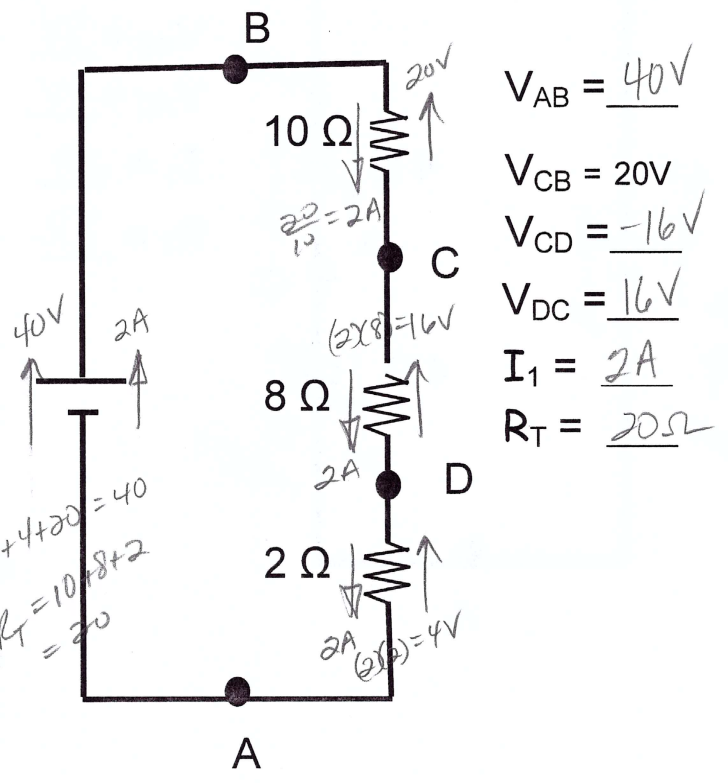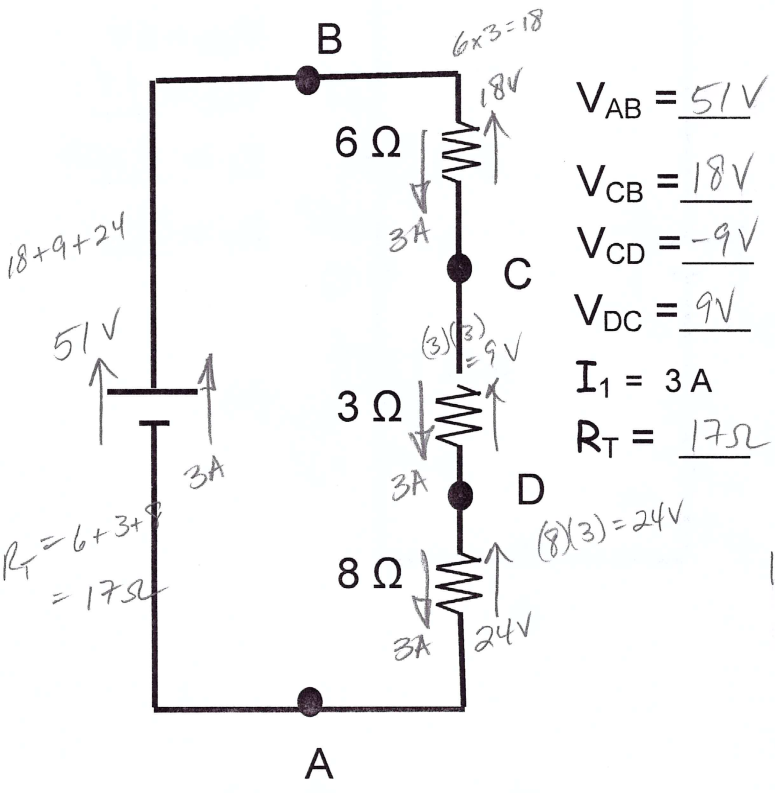

1)

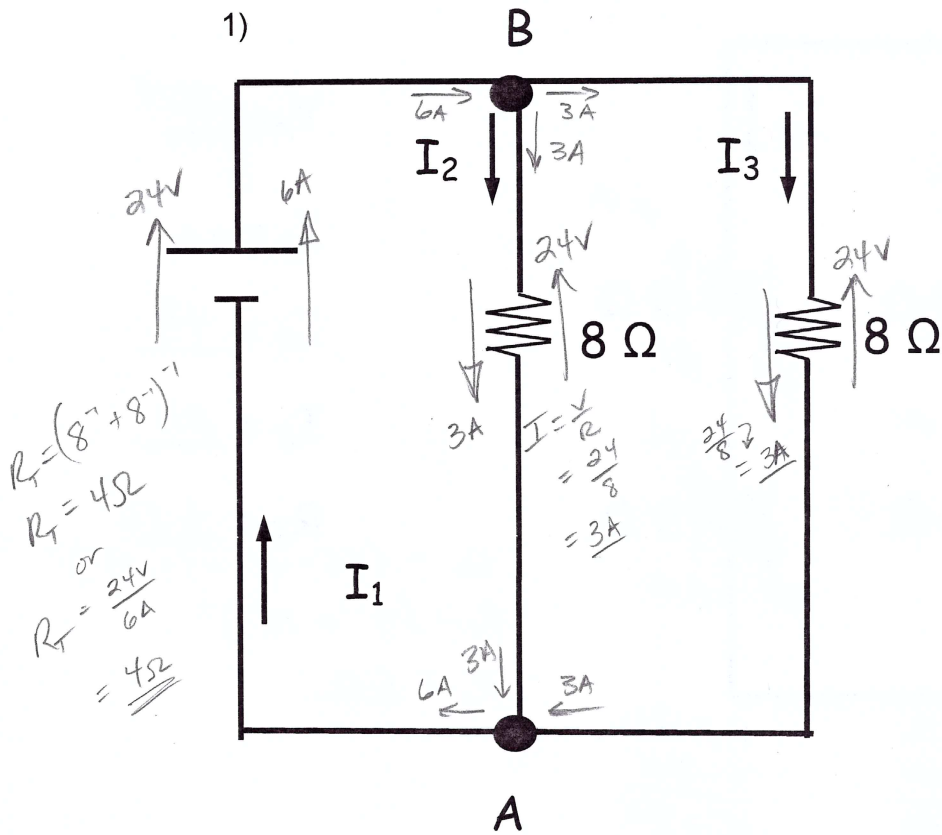

$V_{AB} = 24V$


$I_1 = \underline{6A}$

$I_2 = \underline{3A}$

$I_3 = \underline{3A}$

$R_T = \underline{4\Omega}$

2)

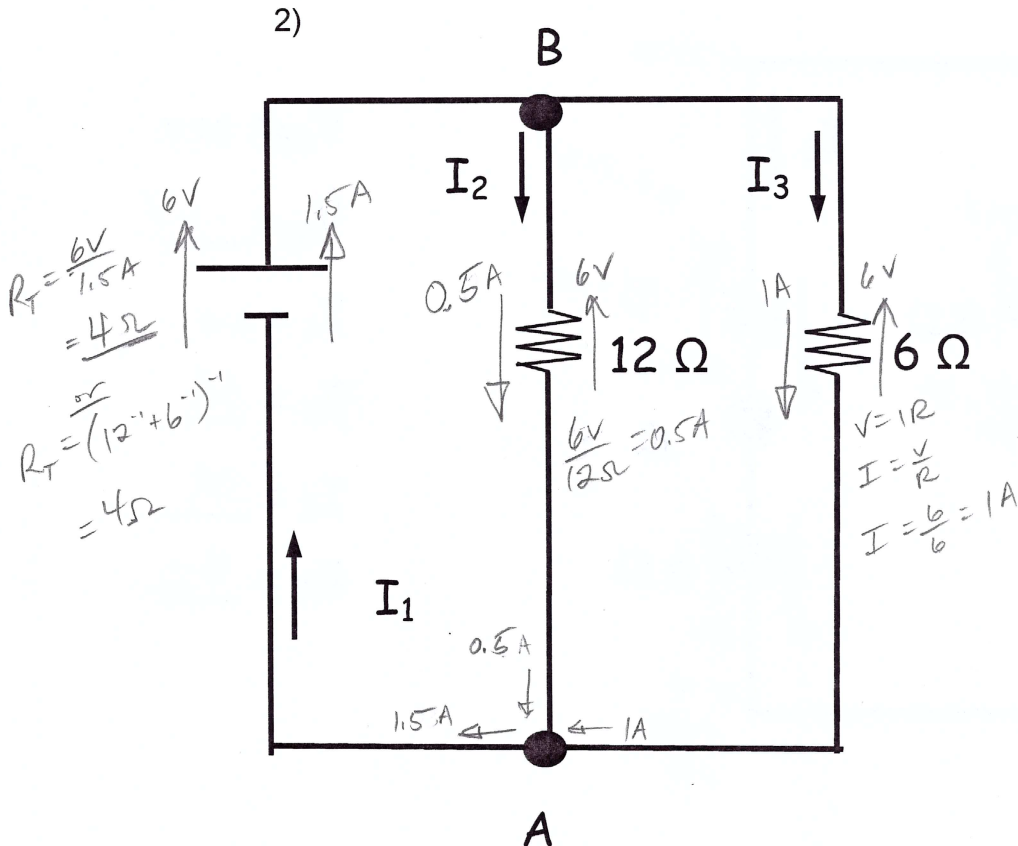


$V_{AB} = 6V$

$I_1 = \underline{1.5A}$

$I_2 = \underline{0.5A}$

$I_3 = \underline{1A}$

$R_T = \underline{4\Omega}$

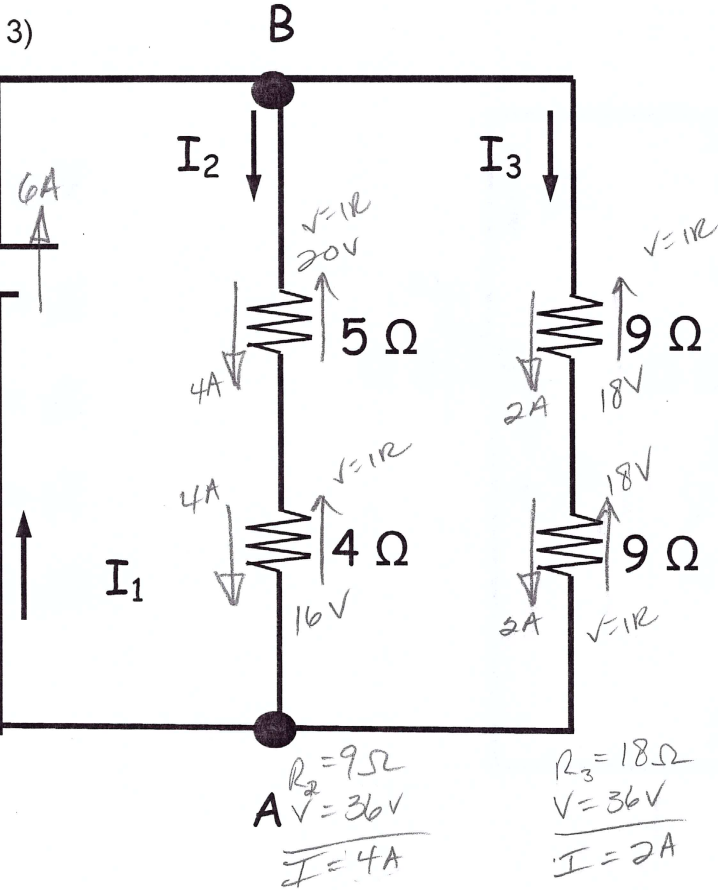

$$V_{AB} = \underline{36V}$$

$$I_1 = 6A$$

$$I_2 = \underline{4A}$$


$$I_3 = \underline{2A}$$

$$R_T = \underline{6\Omega}$$

$$R_T = ((5+4)^{-1} + (9+9)^{-1})^{-1}$$

$$R_T = (9^{-1} + 18^{-1})^{-1}$$

$$R_T = 6\Omega$$

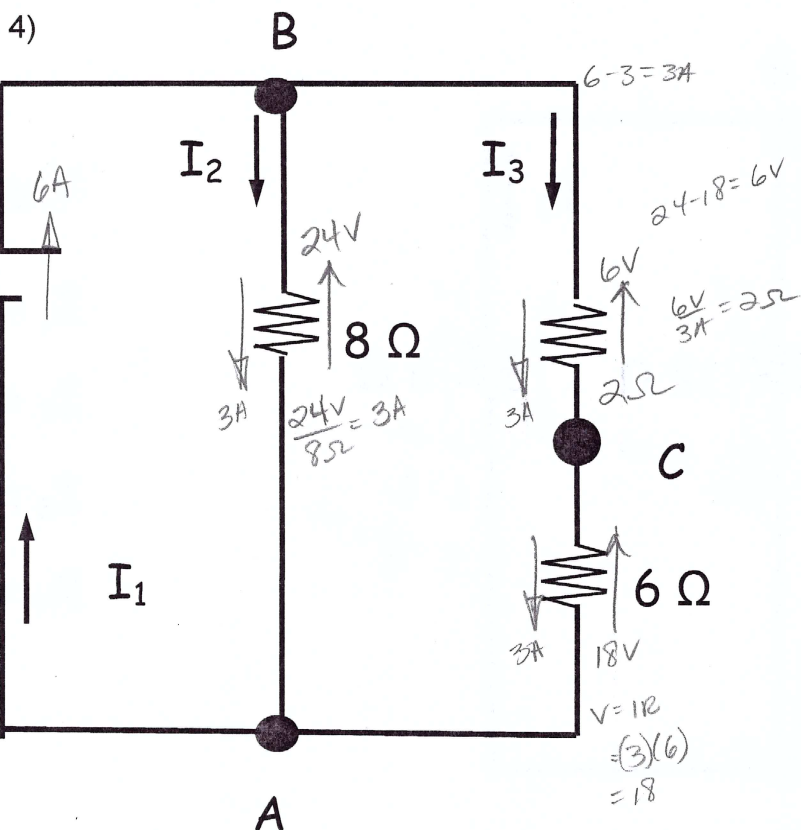

$$V_{AB} = 24V$$

$$V_{BC} = \underline{-6V}$$


$$I_1 = 6A$$

$$I_2 = \underline{3A}$$

$$I_3 = \underline{3A}$$

$$R_T = \underline{4\Omega}$$

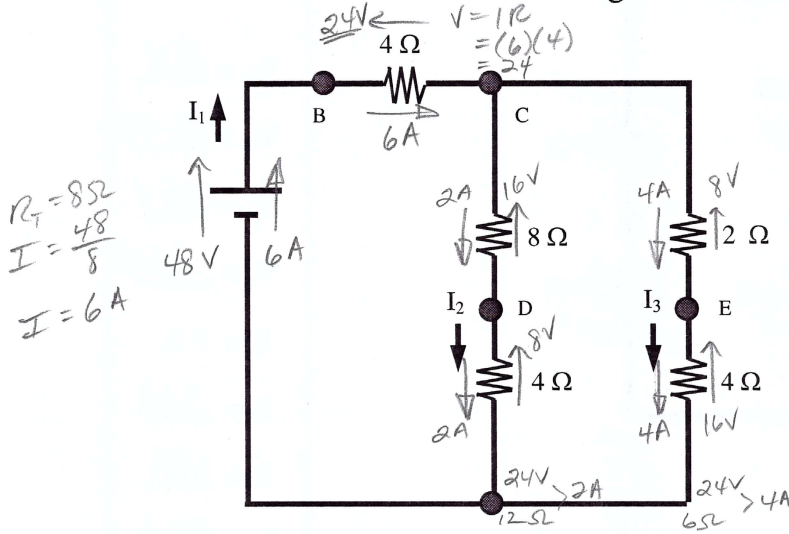
You must show all voltage and current arrows!



$V_{AB} = 48\text{ V}$	$I_1 = \underline{6\text{ A}}$
$V_{CB} = \underline{24\text{ V}}$	$I_2 = \underline{2\text{ A}}$
$V_{AD} = \underline{8\text{ V}}$	$I_3 = \underline{4\text{ A}}$
$V_{EC} = \underline{8\text{ V}}$	$R_t = \underline{8\Omega}$
$V_{AC} = \underline{24\text{ V}}$	

$$R_T = 4 + ((8+4)^{-1} + (2+4)^{-1})^{-1}$$

$$R_T = 8\Omega$$

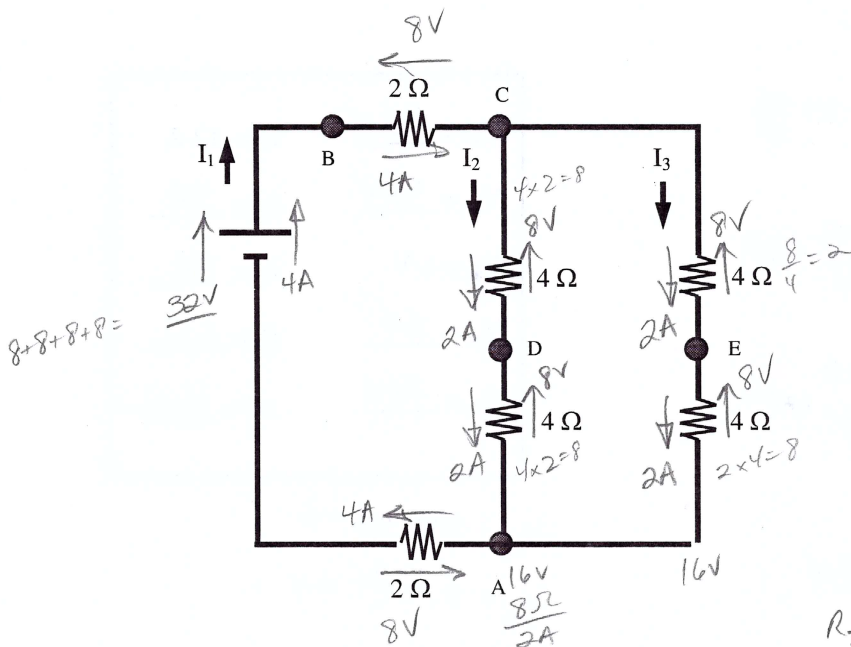

$V_{ab} = \underline{24\text{ V}}$	$I_1 = \underline{4\text{ A}}$
$V_{cb} = \underline{8\text{ V}}$	$I_2 = \underline{2\text{ A}}$
$V_{ad} = \underline{8\text{ V}}$	$I_3 = \underline{2\text{ A}}$
$V_{ec} = 8\text{ V}$	$R_t = \underline{8\Omega}$
$V_{ac} = \underline{16\text{ V}}$	


$$R_T = 2 + ((4+4)^{-1} + (4+4)^{-1})^{-1} + 2$$

$$R_T = 8\Omega$$

$$R_T = \frac{32\text{ V}}{4\text{ A}} = 8\Omega$$


$R_T = 2\Omega$
 $V_{AB} = IR_T = 9(2)$

$V_{ec} = -7.2V + 3.6V$

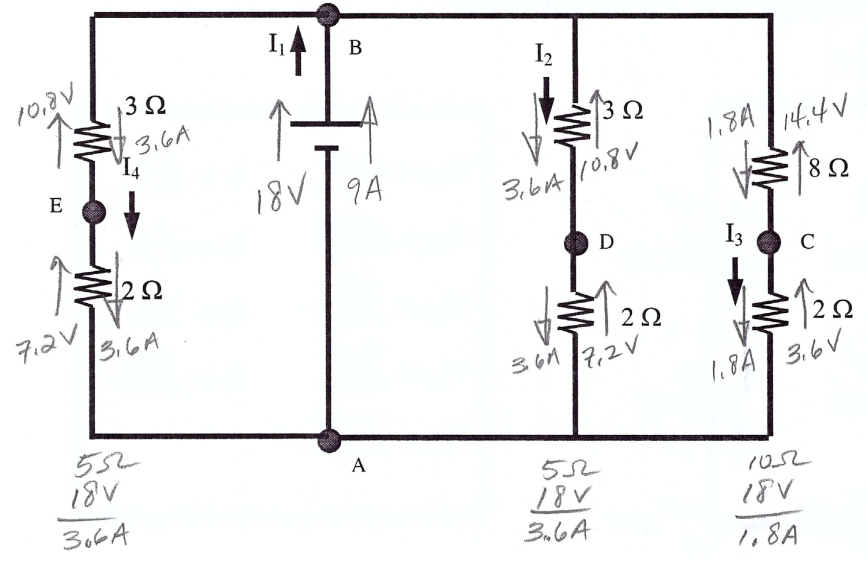

$V_{ab} = 18V$
$V_{cb} = 14.4V$
$V_{ac} = 3.6V$
$V_{ec} = -3.6V$
$I_1 = 9A$
$I_2 = 3.6A$
$I_3 = 1.8A$
$I_4 = 3.6A$
$R_t = 2\Omega$

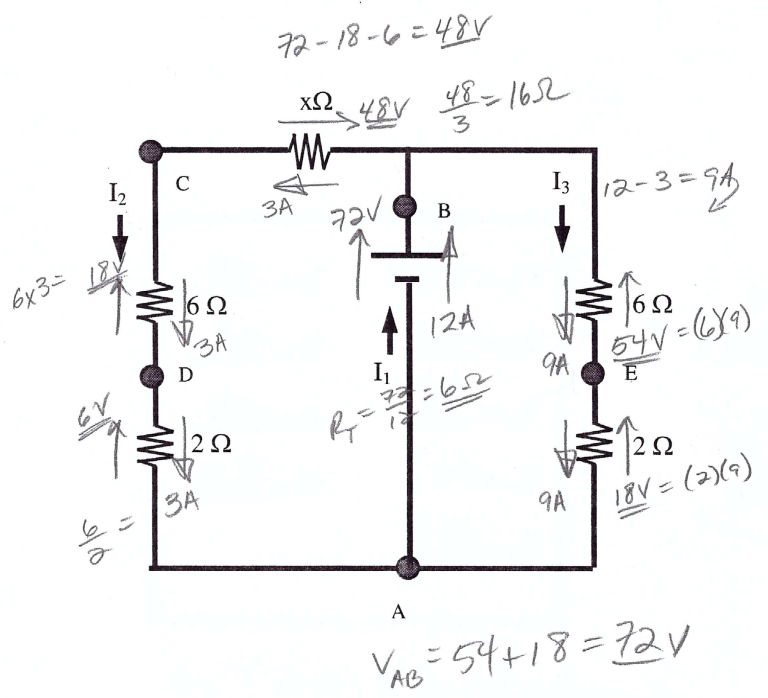$R_T = ((3+2)^{-1} + (3+2)^{-1} + (8+2)^{-1})^{-1} = 2\Omega$



$V_{ab} = 72V$	$I_1 = 12A$
$V_{cb} = 48V$	$I_2 = 3A$
$V_{ad} = 6V$	$I_3 = 9A$
$V_{ec} = 6V$	$R_t = 6\Omega$
$V_{ac} = 24V$	$x\Omega = 16\Omega$

$V_{ec} = 54 - 48 = 6$
 $V_{ac} = 6 + 18 = 24$